

5.4.4. ERZWUNGENE SCHWINGUNG

Reihenschaltung

⇒ inhomogene DGL

$$L\ddot{Q} + R\dot{Q} + \frac{1}{C}Q(t) = U_0 e^{i\omega t} = U(t)$$



$$U(t) = U_0 \cdot e^{i\omega t}$$

Lösungsansatz

$$\begin{aligned} \dot{Q} &= I(t) = I_0 e^{i\omega t} \\ \ddot{Q} &= \dot{I}(t) = i\omega I(t) \\ Q &= \int I(t) dt = \frac{1}{i\omega} I(t) \end{aligned}$$


$$\underbrace{\left(i\omega L + R + \frac{1}{i\omega C} \right)}_{\text{Impedanz!}} I(t) = U(t) \leftarrow$$

Stromamplitude

$$|I(t)| = I_0 = \left| \frac{U(t)}{z} \right| = \frac{U_0}{|z|} =$$

$$= \frac{U_0}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2}}$$

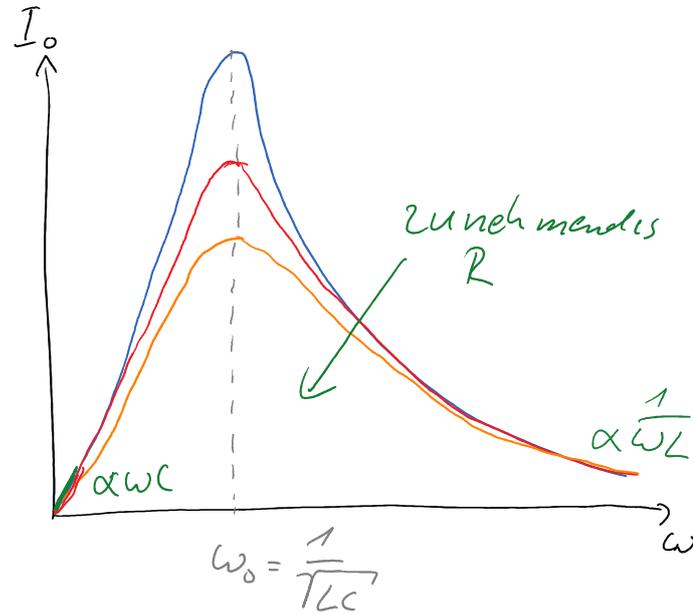kann 0 werden
wenn $\omega L = \frac{1}{\omega C}$
bzw. $\omega_0 = \frac{1}{\sqrt{LC}}$
Resonanzfrequenz




Phasenverschiebung → oben

$$|z| = \sqrt{z z^*}$$

$$I = I_0 \cdot e^{i\omega t}$$

|I|

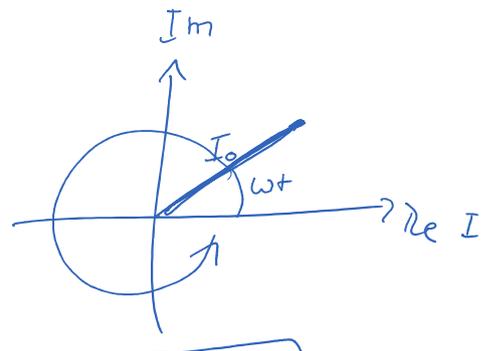

$$I = I_0 \cdot e^{i\omega t} \quad |I|$$

$$|I| = \sqrt{I_0 e^{i\omega t} \cdot I_0 \cdot e^{-i\omega t}} = \sqrt{I_0^2 e^{\underbrace{i\omega t - i\omega t}_{=0}}} =$$

$$= \sqrt{I_0^2 e^0} = I_0$$